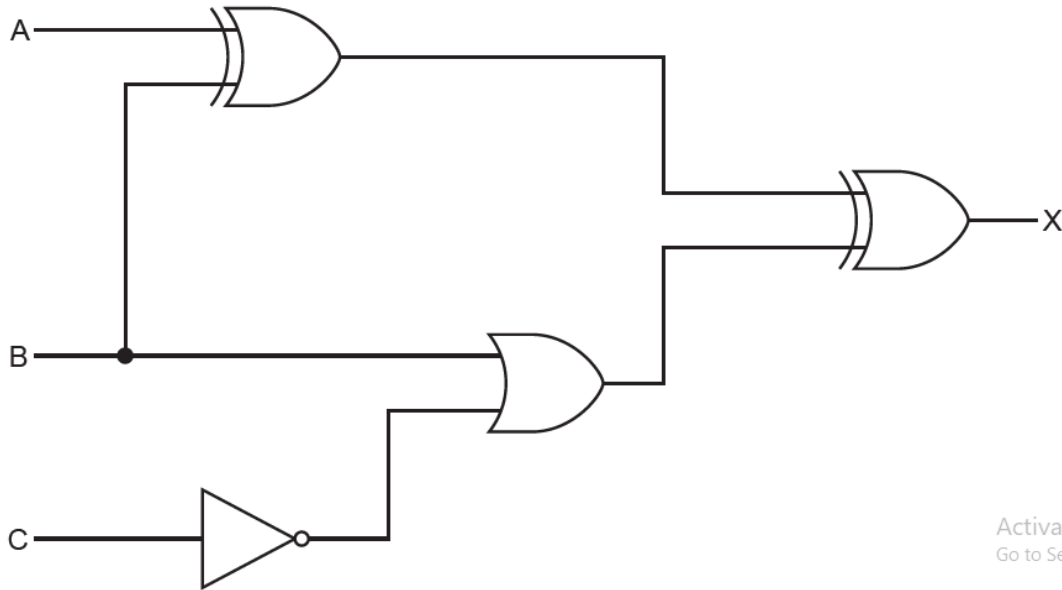


YEAR: MAY/JUNE 2015

(a) Complete the truth table for the following logic circuit:



Activate \n Go to Settin


A	B	C	Workspace	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Activate Win
Go to Settings to

[4]

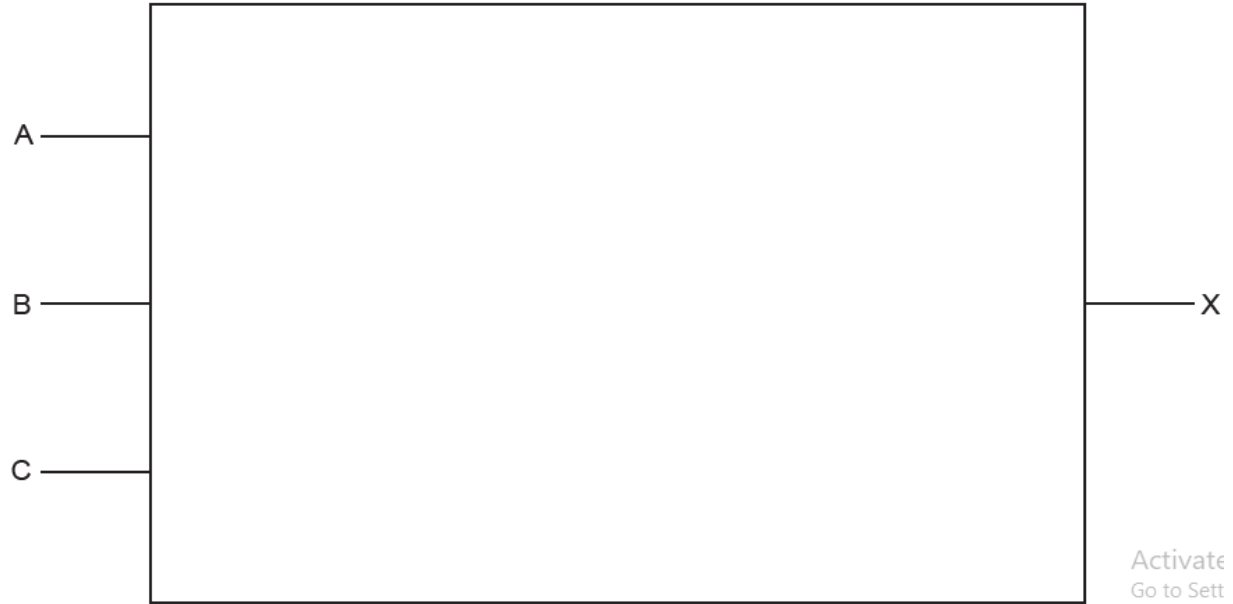
(b) Draw a logic circuit which corresponds to the following logic statement:

$X = 1$ if ((A is NOT 1 OR B is 1) AND C is 1) OR (B is NOT 1 AND C is 1)



Activate
Go to Set

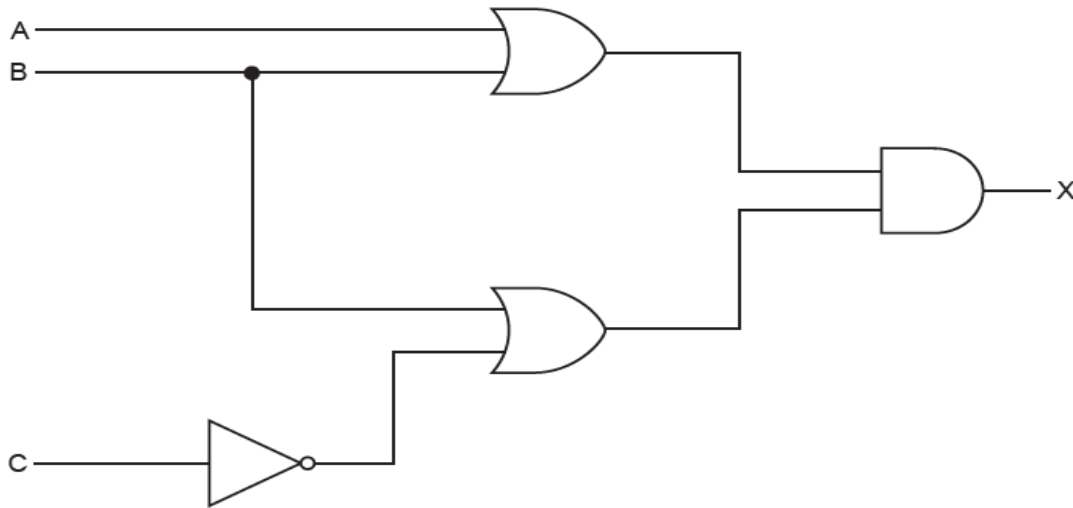(c) Write a logic statement which corresponds to the following logic circuit:



.....

.....

.....

Activ.
Go to S

[3]



A gas fire has a safety circuit made up of logic gates. It generates an alarm ($X = 1$) in response to certain conditions.

Input	Description	Binary value	Conditions
G	gas pressure	1	gas pressure is correct
		0	gas pressure is too high
C	carbon monoxide level	1	carbon monoxide level is correct
		0	carbon monoxide level is too high
L	gas leak detection	1	no gas leak is detected
		0	gas leak is detected

The output $X = 1$ is generated under the following conditions:

gas pressure is correct **AND** carbon monoxide level is too high

OR

carbon monoxide level is correct **AND** gas leak is detected

(a) Draw a logic circuit for this safety system.



[5]



(b) Complete the truth table for the safety system.

G	C	L	Workspace	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]

(c) Complete the truth table for the XOR gate:



A	B	C
0	0	
0	1	
1	0	
1	1	



YEAR: MAY/JUNE 2016

A computer-controlled machine produces plastic sheets. The thickness of each sheet must be within a certain tolerance. The sheets are kept below 50 °C as they move over rollers at 10 metres per second.

Three parameters need to be monitored all the time.

Parameter	Description	Binary value	Conditions
D	sheet thickness	1	thickness of sheet in tolerance
		0	thickness of sheet out of tolerance
S	roller speed	1	roller speed = 10 metres/second
		0	roller speed \neq 10 metres/second
T	temperature	1	temperature < 50 °C
		0	temperature \geq 50 °C


An alarm, X, will sound if:

thickness is in tolerance AND (roller speed \neq 10 metres/second OR temperature \geq 50 °C)

OR

roller speed = 10 metres/second AND temperature \geq 50 °C

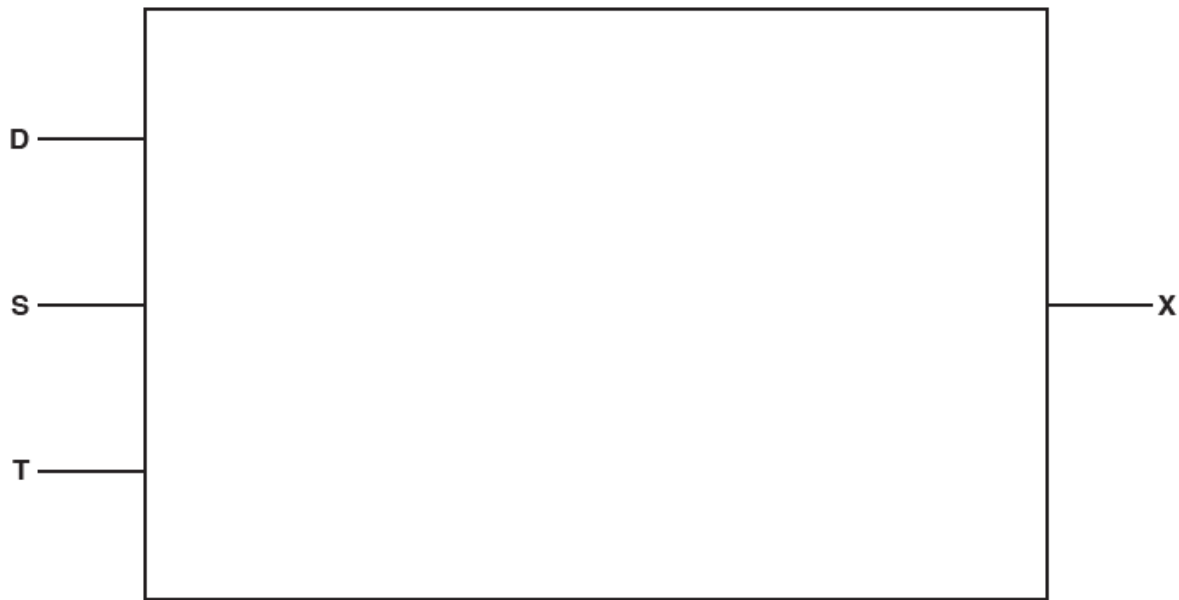(a) Draw a logic circuit to represent the above monitoring system.



[6]


YEAR: MAY/JUNE 2016

(b) Complete the truth table for the monitoring system.

D	S	T	Working Space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]

(a)

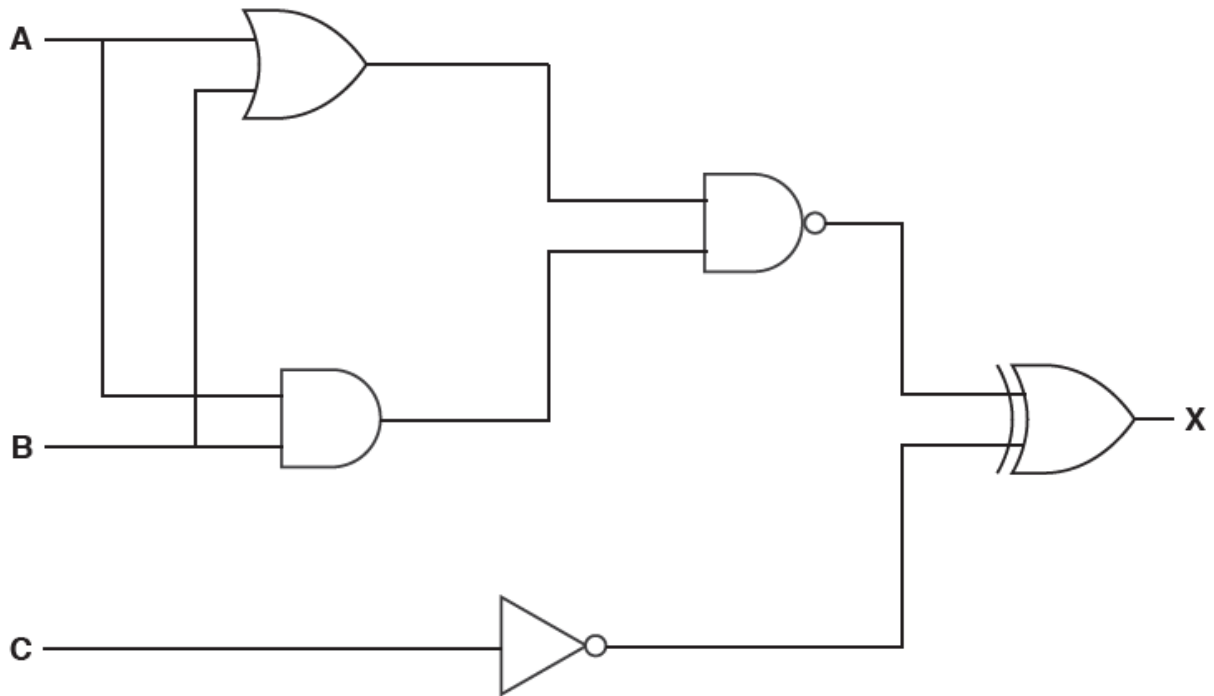


Complete the truth table for this logic circuit.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


[4]

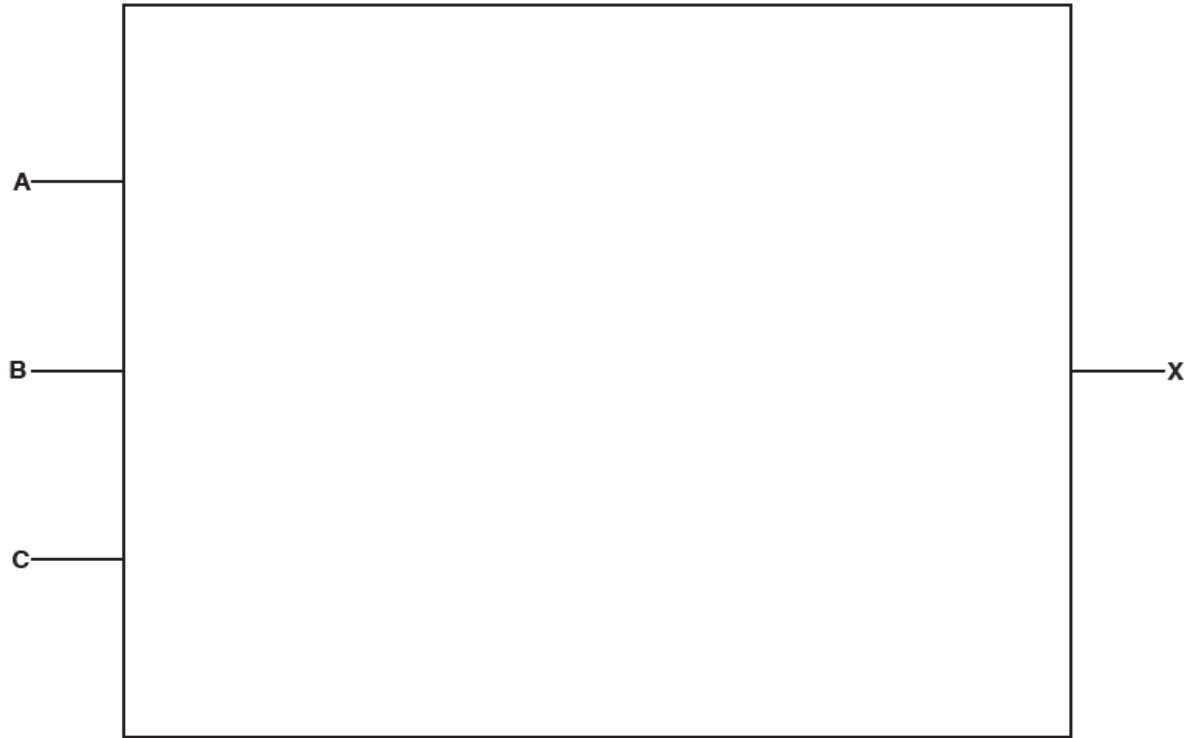(b) Draw a logic circuit corresponding to the following logic statement:

$$X = 1 \text{ if } ((A \text{ is } 1 \text{ OR } B \text{ is } 1) \text{ AND } (A \text{ is } 1 \text{ AND } B \text{ is } 1)) \text{ OR } (C \text{ is NOT } 1)$$




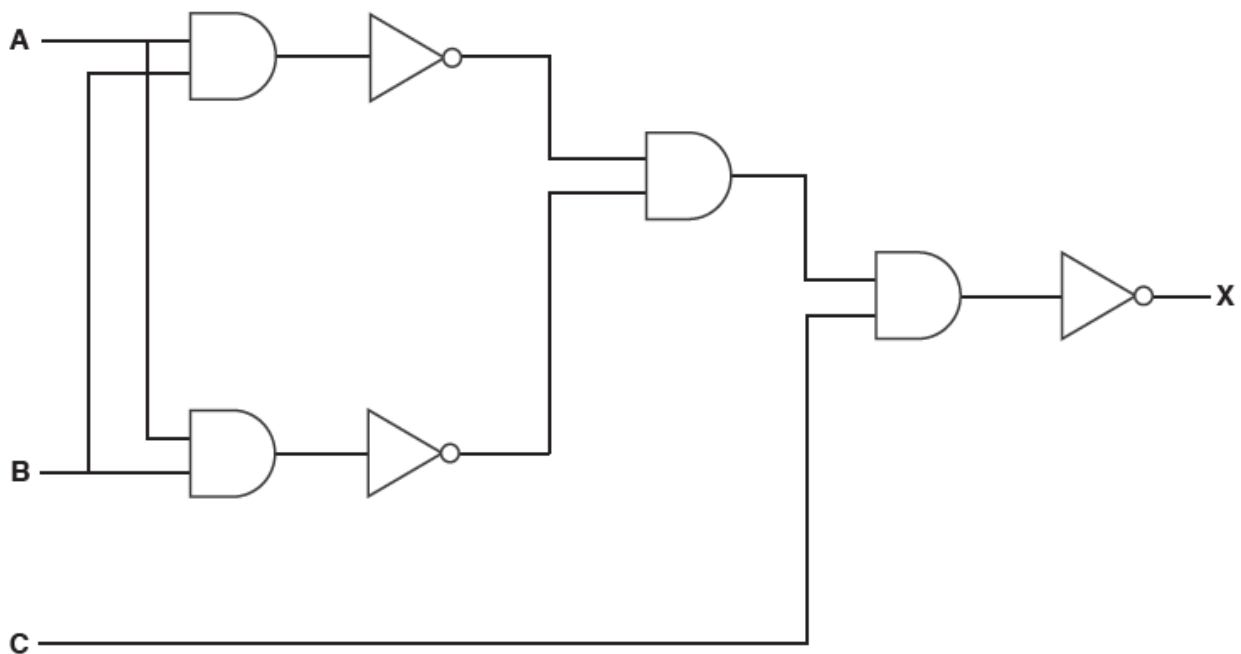(c) Re-draw the following logic circuit using NAND gates only.






Logic circuit re-drawn:

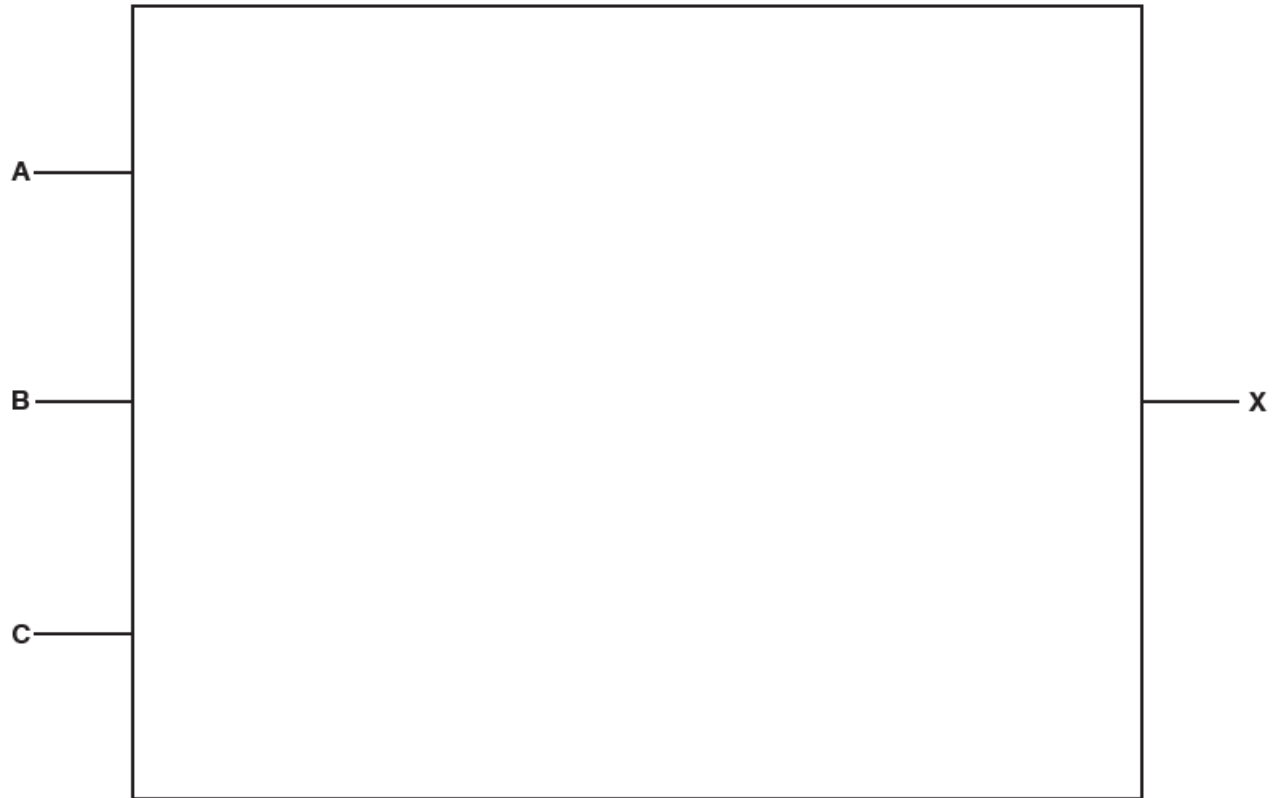

[4]

(a) Complete the truth tables and name the single logic gate that could replace each logic circuit:


(i)

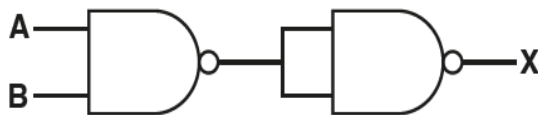

A	B	Working space	X
0	0		
0	1		
1	0		
1	1		

Single logic gate[3]

(ii)

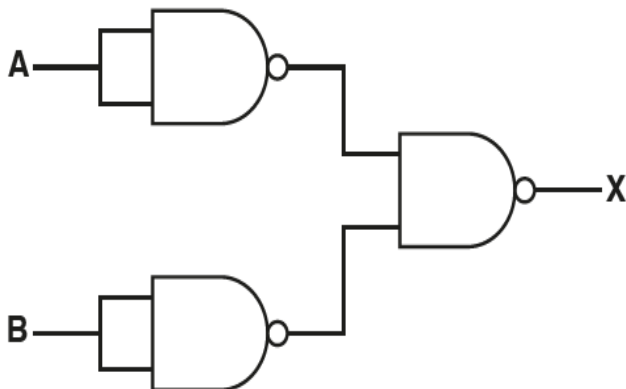

A	B	Working space	X
0	0		
0	1		
1	0		
1	1		


Single logic gate[3]



YEAR: OCT/NOV 2016

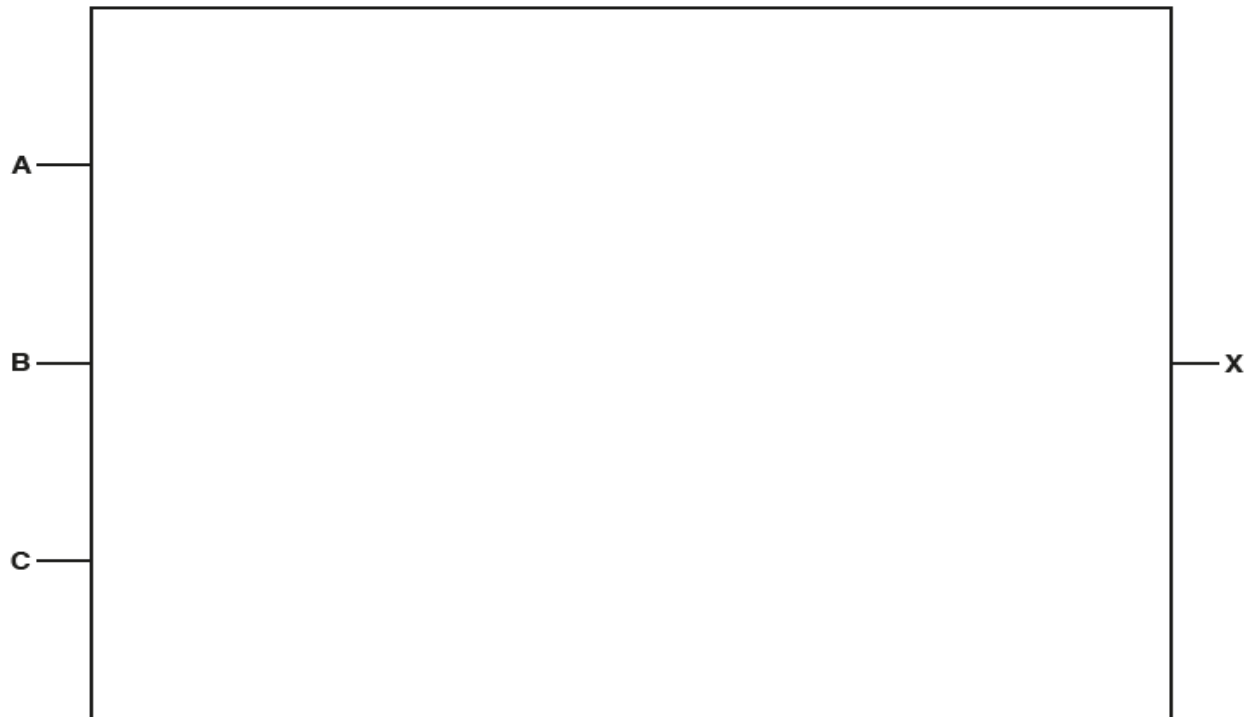(b) (i) Draw a logic circuit to represent the following logic statement:

$$X = 1 \text{ if } (A = 1 \text{ AND } B = 1) \text{ OR } (B = \text{NOT } 1) \text{ AND } C = 1)$$






(ii) Complete the truth table for the logic statement in **part (b)(i)**.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

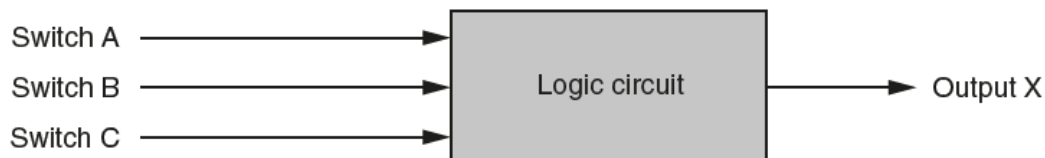Three switches, A, B and C, each send values of 0 or 1 to a logic circuit. Value X is output from the logic circuit.



Output X has a value of 1 depending on the following conditions:


Switch A sends value 1 AND Switch B sends value 0

OR

Switch B sends value 1 AND Switch C sends value 0




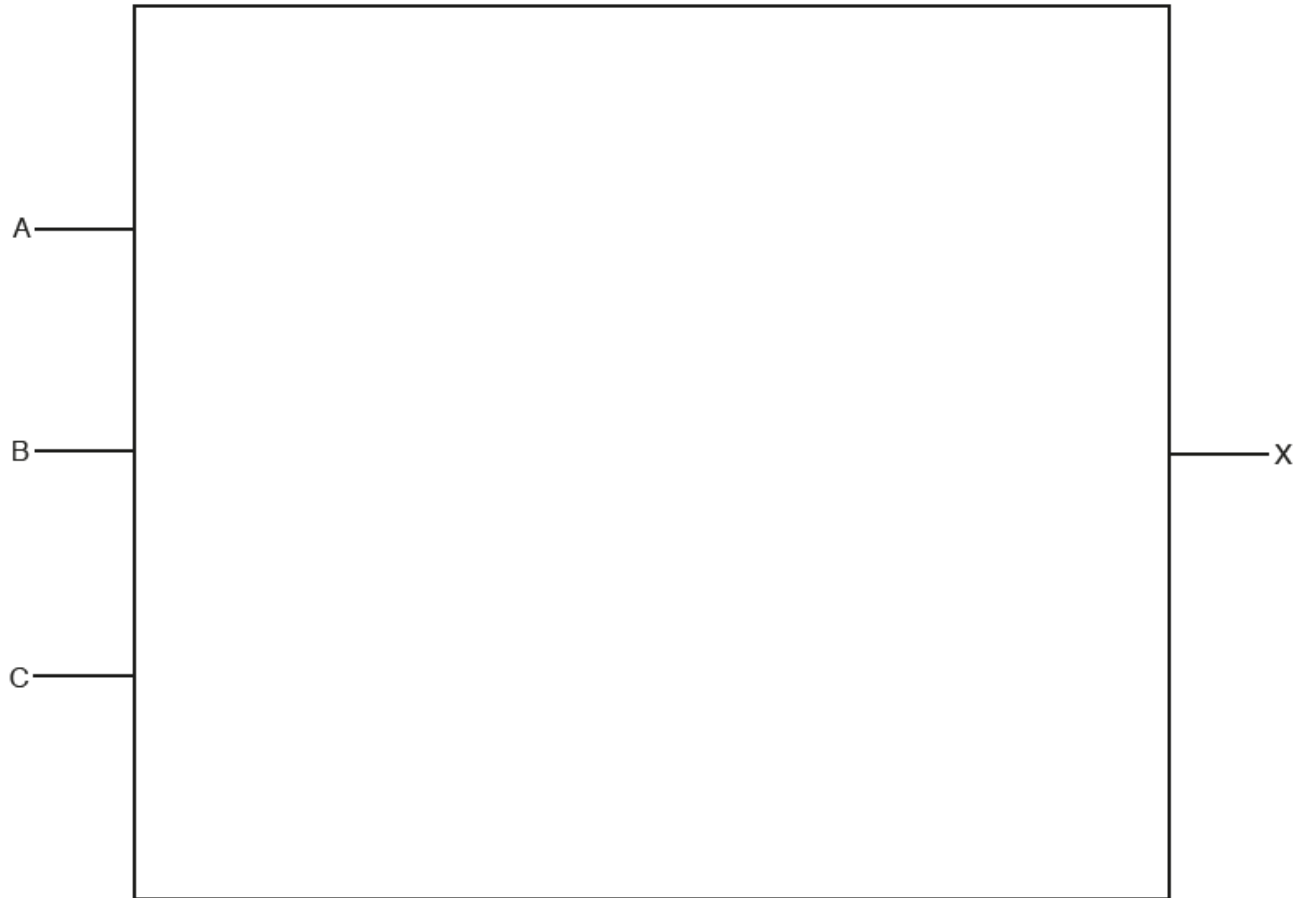(a) Draw a logic circuit to represent the conditions above.



YEAR: MAY/JUNE 2017

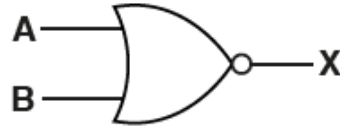
Complete the truth table for the NOR gate.



A	B	Output (X)
0	0	
0	1	
1	0	
1	1	

YEAR: MAY/JUNE 2017

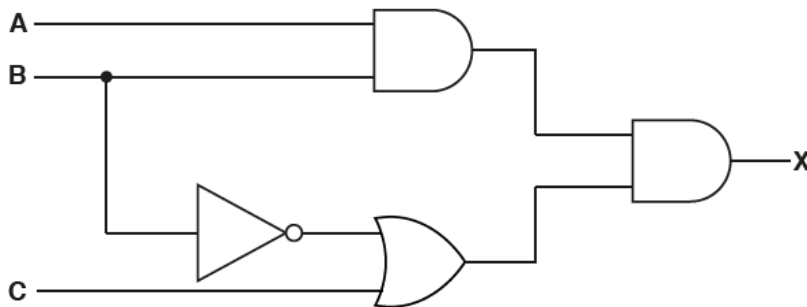Write a logic statement that corresponds with the following logic circuit.



X = [3]

For this logic statement:

$$X = 1 \text{ if } ((A \text{ is } 1 \text{ AND } B \text{ is } 1) \text{ OR } (B \text{ is } 1 \text{ AND } C \text{ is NOT } 1))$$

(a) Draw the logic circuit.



Complete the truth table for the given logic statement.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



For this logic statement:

$$X = 1 \text{ if } ((A \text{ is } 1 \text{ AND } B \text{ is } 1) \text{ OR } (B \text{ is } 1 \text{ AND } C \text{ is NOT } 1))$$

(a) Draw the logic circuit.



[4]

Complete the truth table for the given logic statement.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]

